

Analog Circuit-Blocks for designing an Artificial Neural Network

Pritom Gogoi, Assam Engineering College

June 30, 2021

Abstract

I was able to successfully implement a Gilbert Cell-based multiplier, which is one of the analog circuit blocks required for designing an artificial neural network in the form of an analog computer. The designed multiplier cell is capable of four-quadrant multiplication which is necessary for calculating the product of neuron inputs and the corresponding layer weights. The cell makes use of two levels of differential pairs to divide the tail current, so understanding of differential pairs is key to designing a Gilbert cell multiplier. Apart from its apparent use as a four-quadrant multiplier, it can also be used as a variable gain amplifier, balanced modulator and frequency mixer.

2 Implemented Circuit

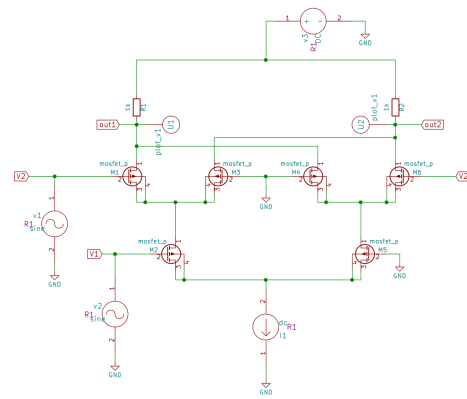


Figure 1: Implemented circuit diagram.

1 Circuit Details

In course of the event, I successfully designed and simulated the working of a Gilbert cell-based multiplier that can be used as a circuit block when designing an analog equivalent of an artificial neural network. In order to work as a four-quadrant multiplier, the multiplier output, V_{out} has to follow the equation $V_{out} = K \cdot V_1 \cdot V_2$, the constant K depends on the configuration of the circuit. It is to be noted that in order to be able to achieve outputs close to the theoretical value, the PMOS devices used should be near identical.

The multiplier works by using two levels of cascaded differential pairs, the tail current I_1 at the bottom (which maybe replaced by a PMOS) is divided by a differential pair formed by M_2 and M_5 . V_1 is fed into the gate of these two devices. The divided tail currents then reach one of the two differential pairs (M_1 - M_3 or M_4 - M_6), one difference at this level is that the input V_2 at the gates of these PMOS devices are cross-connected as shown in the circuit schematic. Finally, the divided tail currents reach the resistors where we obtain the output voltage V_{out} by calculating the difference between the voltage drops across resistors R_1 and R_2 .

The plotted waveform on the left shows the sinusoidal inputs V_1 and V_2 , while that on the right is the plot for V_{out} . We can notice that the value of V_{out} reaches zero when one (or both) of the inputs are zero. It is evident that the output waveform follow the rules of multiplication in all quadrants. The waveform described in the literature survey could not be replicated due to the limitations of ngspice.

3 Implemented Waveforms

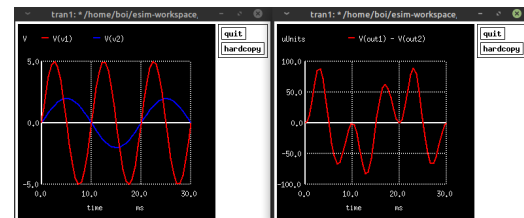


Figure 2: Implemented waveform.

References

- [1] B. B. I. Fikret Basar Gencer, Xhesila Xhafa and M. B. Yelten. Design of an analog circuit-based artificial neural network. <https://ieeexplore.ieee.org/abstract/document/8990559>.
- [2] B. Gilbert. The gilbert cell, the linear mixer with gain, in cmos or bipolar. <https://ieeexplore.ieee.org/document/6499939/>.
- [3] W2AEW. Basics of the gilbert cell | analog multiplier | mixer | modulator. <https://www.youtube.com/watch?v=7nmmb0pqTU0>.